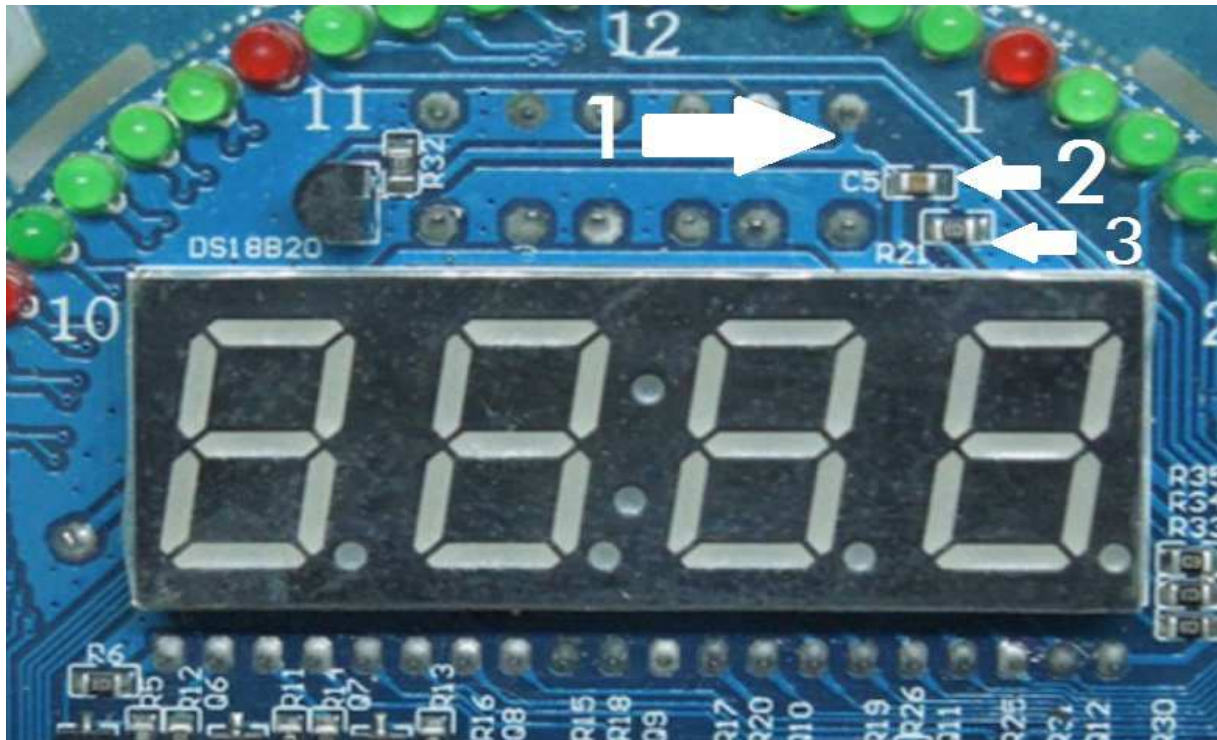


## Modifications of the EC1204B board to use with an Atmel ATmega8515 or ATmega162:



Many, many thanks to Cristian Copcea , who described the necessary hardware changes in his blog.  
(<http://blog.copcea.ro/?p=1252>)



- 1)
  - a) Cut wiring on PCB, removing the link from the reset switch to VCC.
  - b) Solder a piece of wire linking the reset switch to GND.
- 2) Desolder C5.
- 3) Desolder R21. Solder R21 at the place of C5, building a pull-up resistor for the reset pin.

IMPORTANT: Do not solder anything at the place of R21. A capacitor on the reset pin will make the processor unprogrammable through ISP (in-system programming), since the RST signal is handled by the programmer.
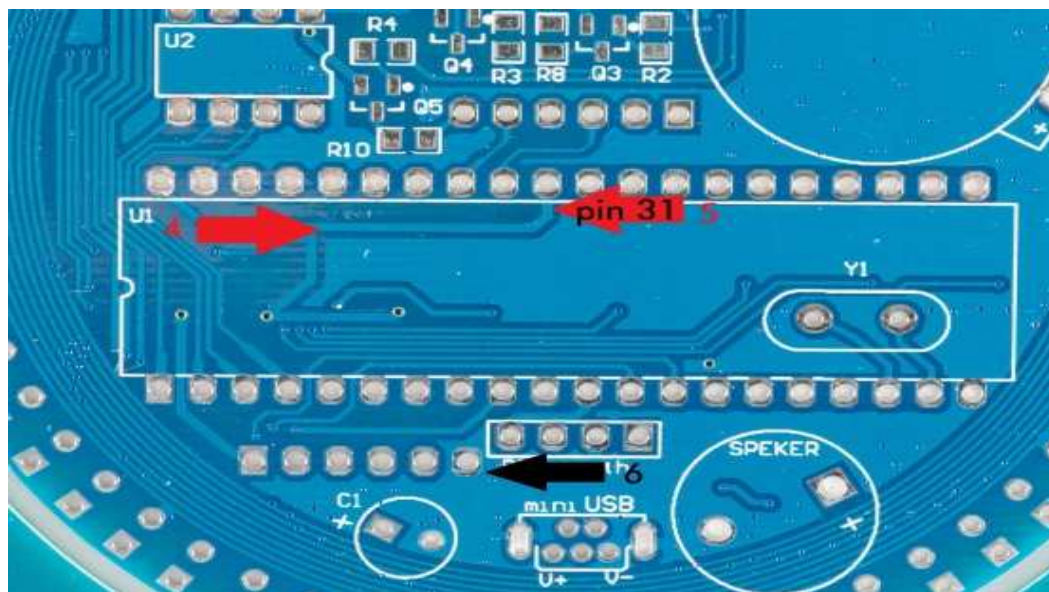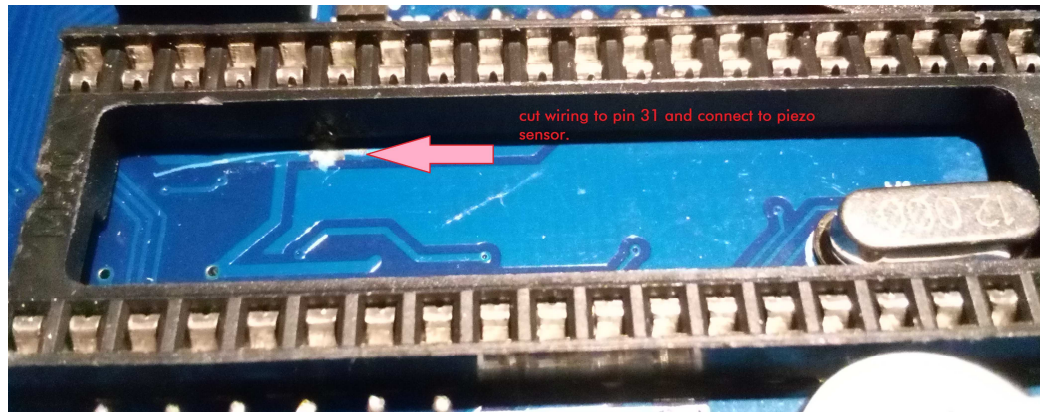
## Modifications of the EC1204B board to use INT2 (pin31 of ATmega8515) as input for the nerf gun target detection:



- 4) Cut wiring on PCB, removing the link from VCC to Pin 31 of  $\mu C$ .
- 5) Solder the positive wire of the piezo stuff to Pin 31 of  $\mu C$ .
- 6) Solder GND of piezo stuff to GND of PCB.

Piezo schematic:

